



# CE/CZ 3001: Advanced Computer Architecture

**(Module 3: Data-path and Control Design)**

Dr Smitha K. G.  
School of Computer Science  
And Engineering

# Topics covered till now

- LEGv8 ISA:

- Instruction format
  - R-format, D-format, I-format, CB format and B-format
- Addressing modes
  - Register addressing
  - Base addressing
  - Immediate addressing
  - PC-relative addressing
- Functionality
  - ALU instructions
  - Data transfer instructions
  - Conditional and unconditional instructions


# Outline

- Review of basic logic devices and register file
- Single-cycle datapath design

# Basic datapath components

 
## Arithmetic and logic unit (ALU)

- ALU - is the CPU's data processing or execution unit
  - implements fixed point operations.
- The floating point and complex numerical functions are performed by arithmetic co-processors
- Typical arithmetic functions:  
Add, subtract, multiply, divide.
- Logic functions: AND, OR, XOR, and NOT.
- Other data manipulation functions:  
Arithmetic and logical shifts, incrementing and decrementing the operands etc.


 
# Arithmetic and logic unit


- $n$ -bit ALU can be made by placing  $n$ -1-bit ALU slices in parallel
- The function select ( $F0..Fn$ ) for each 1-bit ALU is driven by the instruction being executed.



$$R = A \text{ op } B$$
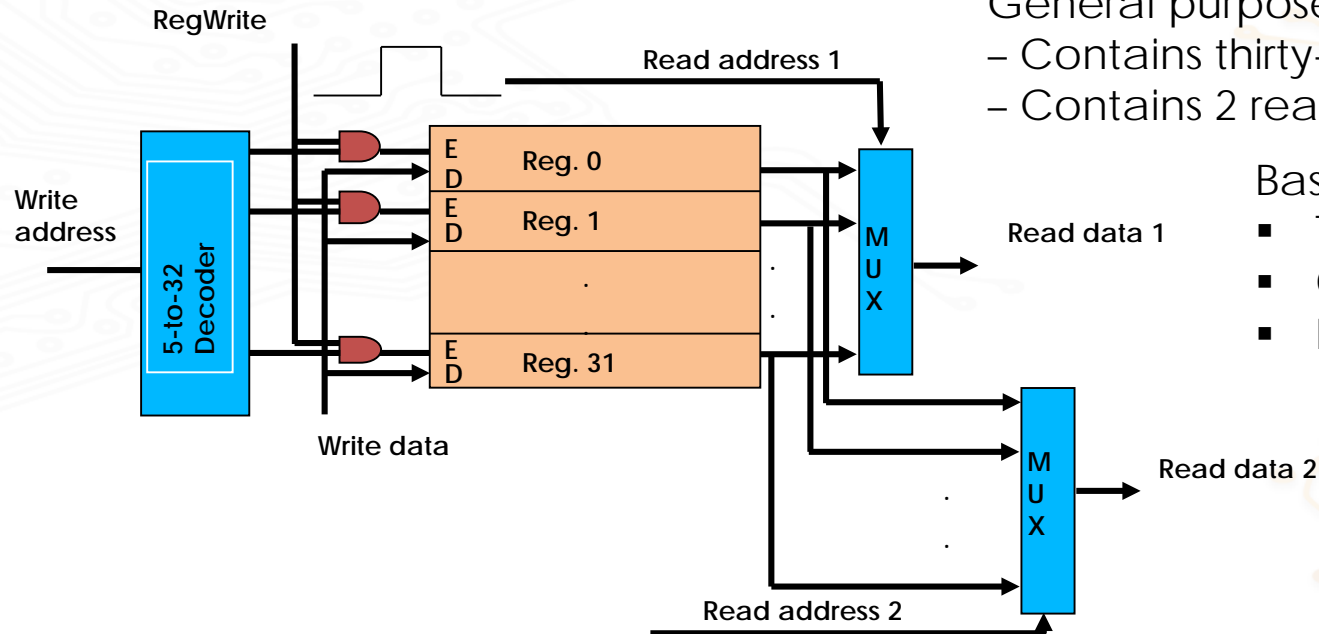
# Register File

A register file is a collection of registers in which any register can be read or written by specifying the address. They form the temporary storage inside the CPU.



General purpose register (GPR) file

- Contains thirty-two 64-bit registers
- Contains 2 read ports and 1 write port


Basic building blocks

- Two 32:1 Multiplexor
- One 5 to 32 Decoder
- Register using Flipflop

# Building blocks of Register File (Part 1/3)
 
## Multiplexer:

The multiplexer used is 32:1 MUX in MIPS register file. But for explanation we are using 4:1 MUX. A 4: 1 MUX selects one of the 4 inputs according to value of the select line (CS)




CS	Output
00	I0
01	I1
10	I2
11	I3

# Building blocks of Register File (Part 2/3)
 
## Decoder:

The decoder used is 5 to 32 decoder in register file. But for explanation of a decoder we are using 2 to 4 decoder.

- A decoder having  $n$  input bits will have  $2^n$  output bits.
- Only one output of a decoder is high at any given time depending on input.
- Output of the decoder "L0, L1, L2 and L3" can be used with **RegWrite signal** of a register file to write to the register file.





input	L0	L1	L2	L3
00	1	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1





  
# Write and read port of MIPS Register File



Read Ports for a Reg. File
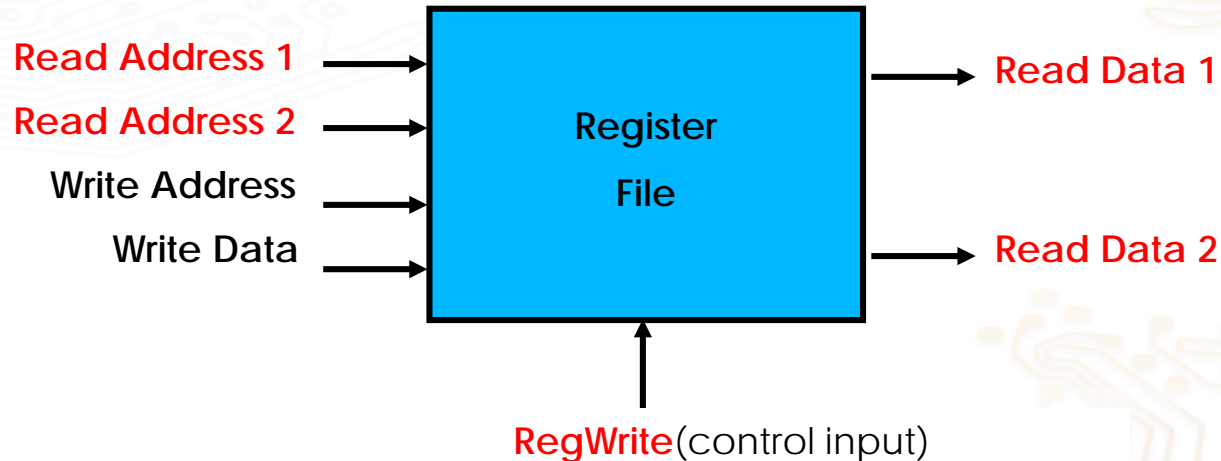
# Register File

- Consists of a set of registers that can be read and written by supplying a register number to be accessed
- Can be implemented with a multiplexer for each read and a decoder to write and array of registers built from D-FF




# Working of Register File

- Ex: ADD X31, X1, X0
- Read address1=1=00001
- Read address2=0=00000
- Write address=31=11111
- Assume Value inside

Reg. 0=0 and  
Reg. 1 =5

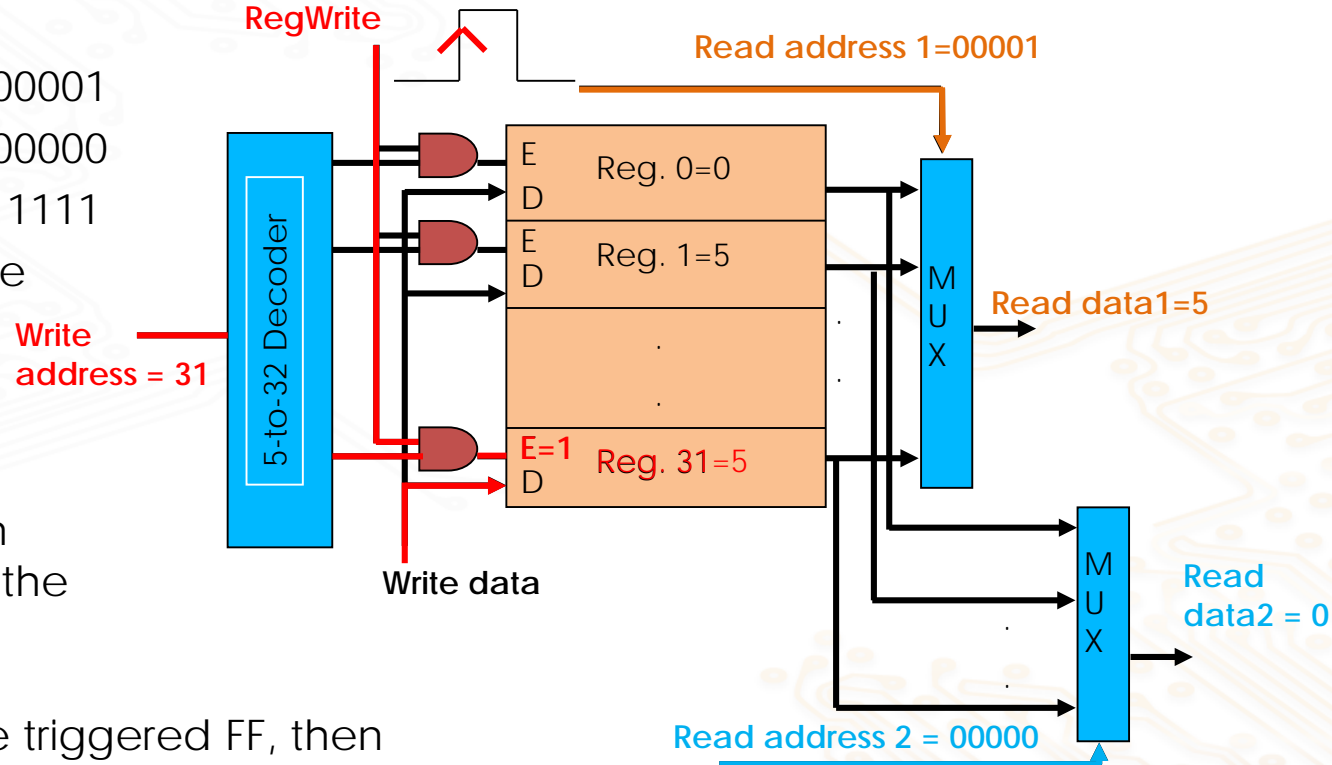- Do note that write happens only when  $\text{RegWrite}=1$  and at the edge of the clock.
- So if it is a +ve edge triggered FF, then write occurs only at the positive edge of clock.




# What happens when same register is read and written during same clock cycle?

- The register read happens combinational (no clock).
- The register will be valid during the time it is read.
- The value returned will be the value written in the earlier clock cycle.
- The write of the register file occurs on the clock edge.
- If we want to read to return the value currently being written- we need additional logic.

 
# Introduction to datapath – Instruction fetch (Part 1/3)

- Instruction Memory: Memory to store the instructions of program and supply instructions given an address.
  - Needs only a read access
  - Treated as a combinational logic (output at any time reflects the contents of the location specified by the address input)
  - No read control signal is needed



 
# Introduction to datapath – Instruction fetch (Part 2/3)

- Program Counter (PC): Register that holds the address of the address of current instruction.
  - Register that is written at the end of every clock cycle



 
# Introduction to datapath – Instruction fetch (Part 3/3)

- First, fetch the current instruction from instruction memory using PC.
- Second, prepare for the next instruction.
  - By incrementing PC by 4 to point to next instruction 4 bytes later





 
# Datapath for R type instructions: (register addressing)




- **R-type** or (Register format)- All data values (operands/results) are located in registers and addressing mode is **Register addressing**
- The instruction is read from instruction memory (IF)
- The source registers specified by fields **Rn** and **Rm** of the instruction are read from the register file, and fed to the ALU (ID)
- ALU performs the operation specified in the opcode (EXE)
- The result is stored in the destination register, specified by field **Rd** of the instruction (WB)
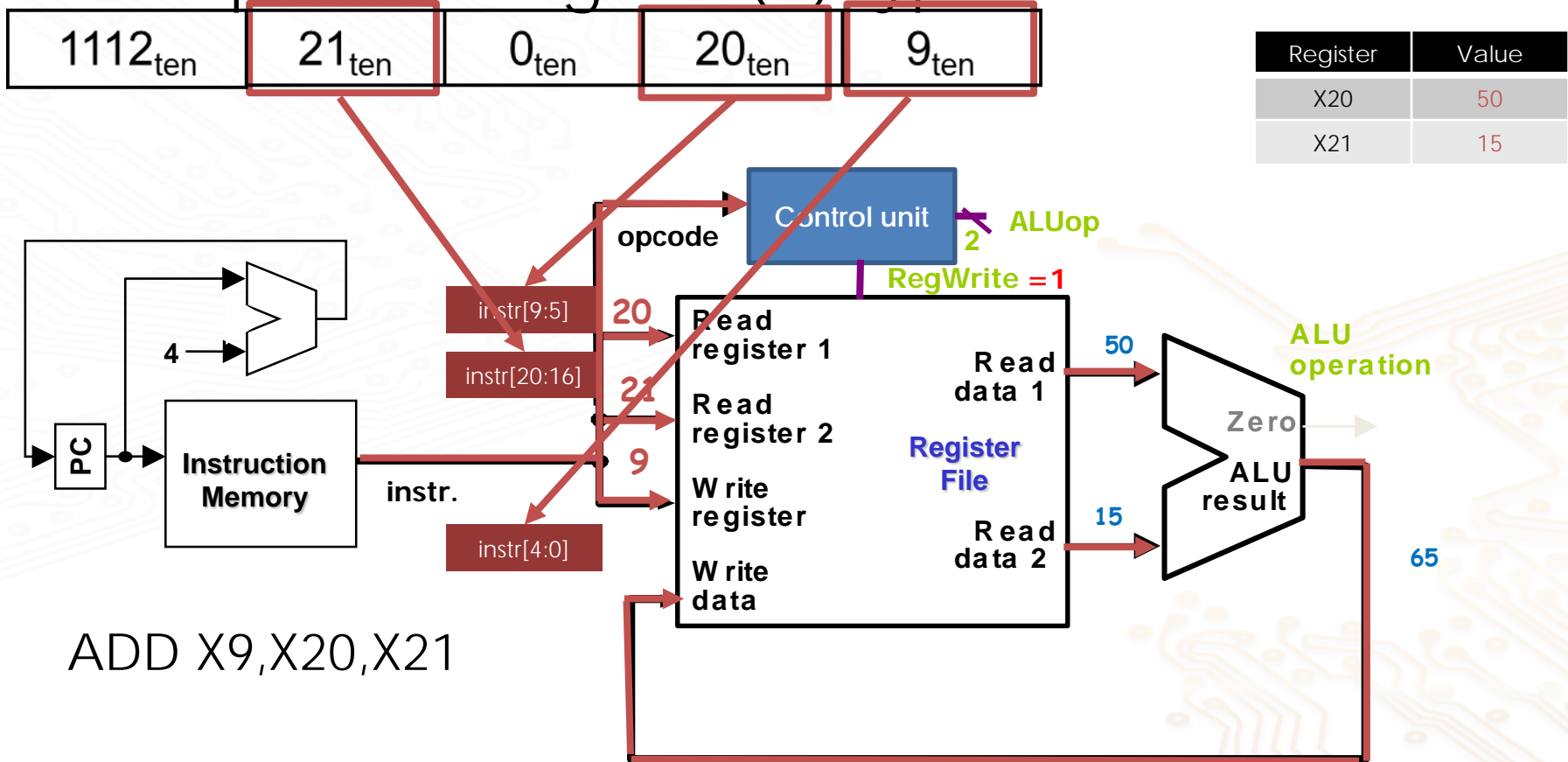
# Datapath of Register (R) type instruction



 
# Data transfer (D)type – Memory related instructions (Part 1/4)



- Memory access instructions: **LDUR** and **STUR**
- **LDUR Rt, [Rn, #address]**
  - Source register specified by field “**Rn**” is read from register file, and fed to ALU with “**address**” after sign-extension to 64-bits
  - ALU calculates the memory address of word to be loaded (EXE)
  - Content of the memory at location specified by the calculated address is read (MEM)
  - Word read from memory is loaded to the register specified by the address in “**Rt**” (WB)
 
# Data transfer (D)type – Memory related instructions(Part 2/4)




## ■ STUR Rt, [Rn, #address]

- The field "**Rt**" in this case contains the address of the register that has the value to be stored: (while in case load instructions "**Rt**" was used as write address )
- "**Rt**" is used as read address-2 for STU
- The source register specified by "**Rn**" is read from register file, and fed to ALU with the sign extended operand "**address**" to calculate the address of memory location
- ALU calculates the address of memory location where the data is to be stored (EXE)
- Result is stored at the memory location whose address is calculated by the ALU (MEM)
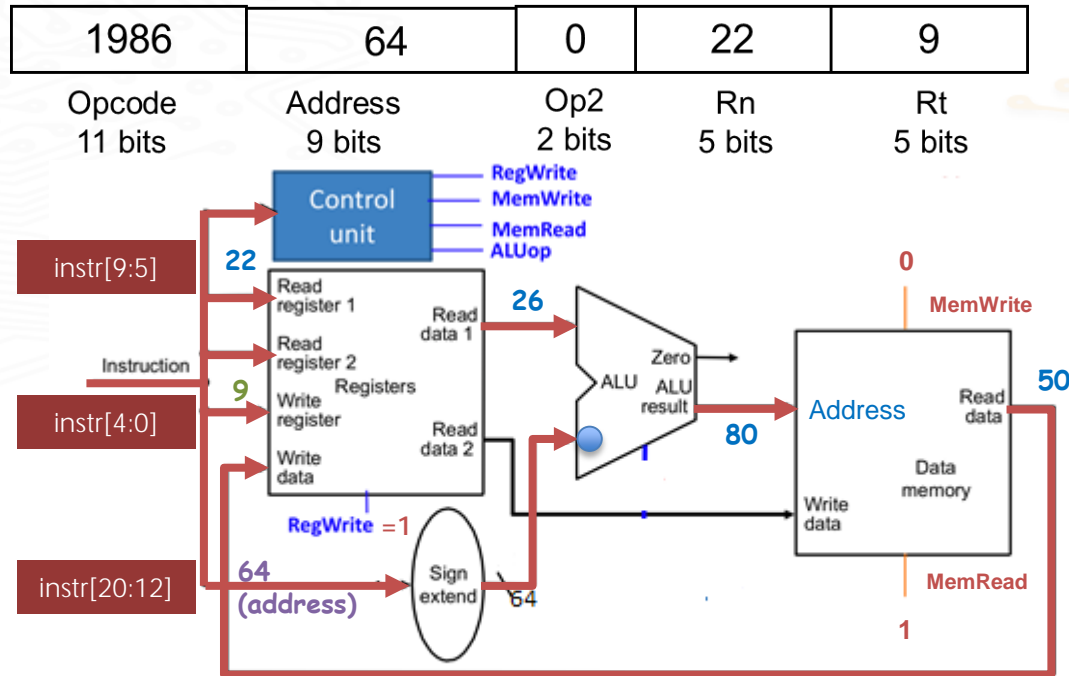
# Data transfer (D)type – Base addressing Part 3/4

- Operation **LDUR Rt, [Rn, #address]**
- LDUR X9, [X22, #64] //  $[X9] \leftarrow \text{mem}[[X22] + 64]$




Register	Value
X22	26

Memory[80]
50
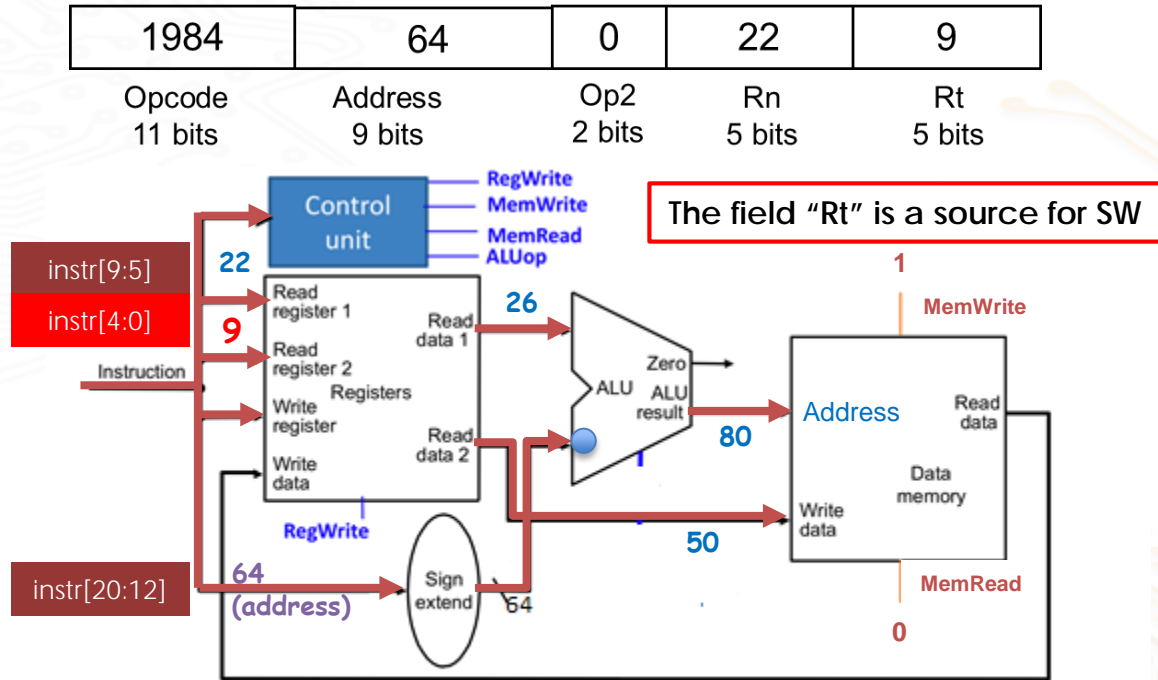
# Data transfer (D)type – Base addressing Part 4/4

- Operation **STUR Rt, [Rn, #address]**
- STUR X9, [X22, #64] // [X9]  $\rightarrow$  mem[[X22] + 64]




Register	Value
X22	26
X9	50

Memory[80]
50
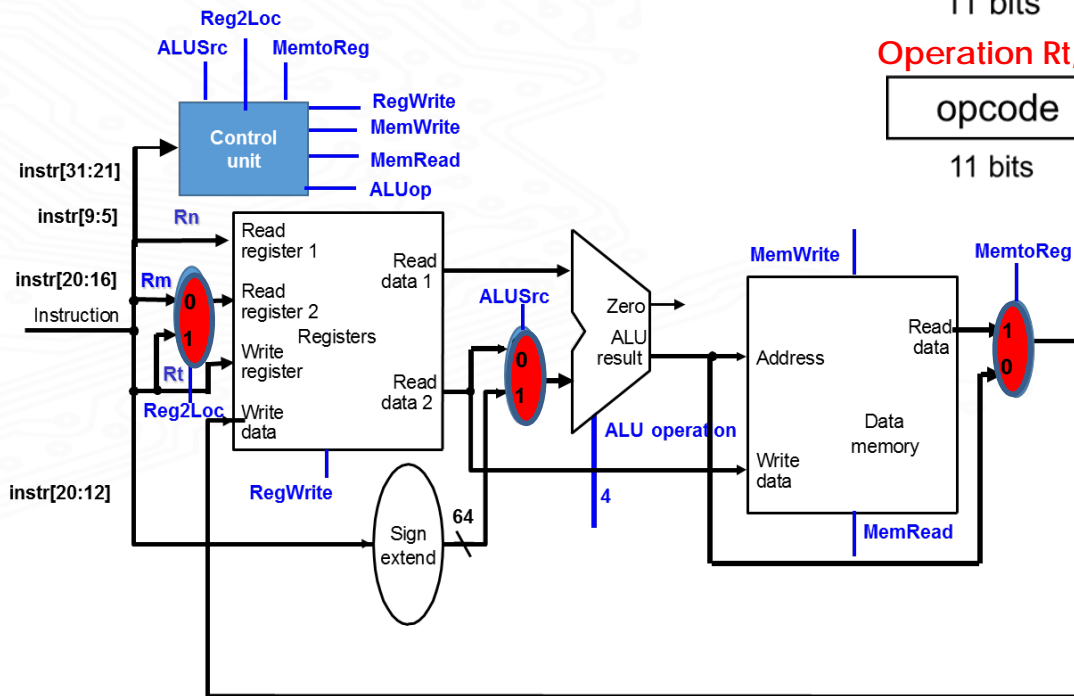
# Datapath for R and D-type Instructions

How can we combine the data path for R and D type instructions?



Operation Rd, Rn, Rm

opcode	Rm	shamt	Rn	Rd
11 bits	5 bits	6 bits	5 bits	5 bits

Operation Rt, [Rn, address]

opcode	address	op2	Rn	Rt
11 bits	9 bits	2 bits	5 bits	5 bits


“Rn” -Source for R and D type  
 “Rd” -Destination for R-type  
 “Rt” -destination/source for D-type

Extra mux needed


“Reg2Loc” -Selects between “Rt” and “Rm” as the source register address  
 “ALUSrc” -Selects between “read data2” and “address” as the source to ALU  
 “MemtoReg”-select the result from memory or from ALU
 
# Datapath for I type instructions: (Immediate addressing)

- **I-type** or (Immediate format)- one data in immediate field
- **immediate addressing**: Read from the register and immediate field and write to register




 - Immediate field is zero-extended
- Opcode is reduced to 10 bits to have more range for immediate field.
- Example: ADDI X1, X2, #50 ( $[X1] \leftarrow [X2] + 50$ )





 
# Datapath for I type – Immediate addressing




Register	Value
X2	30

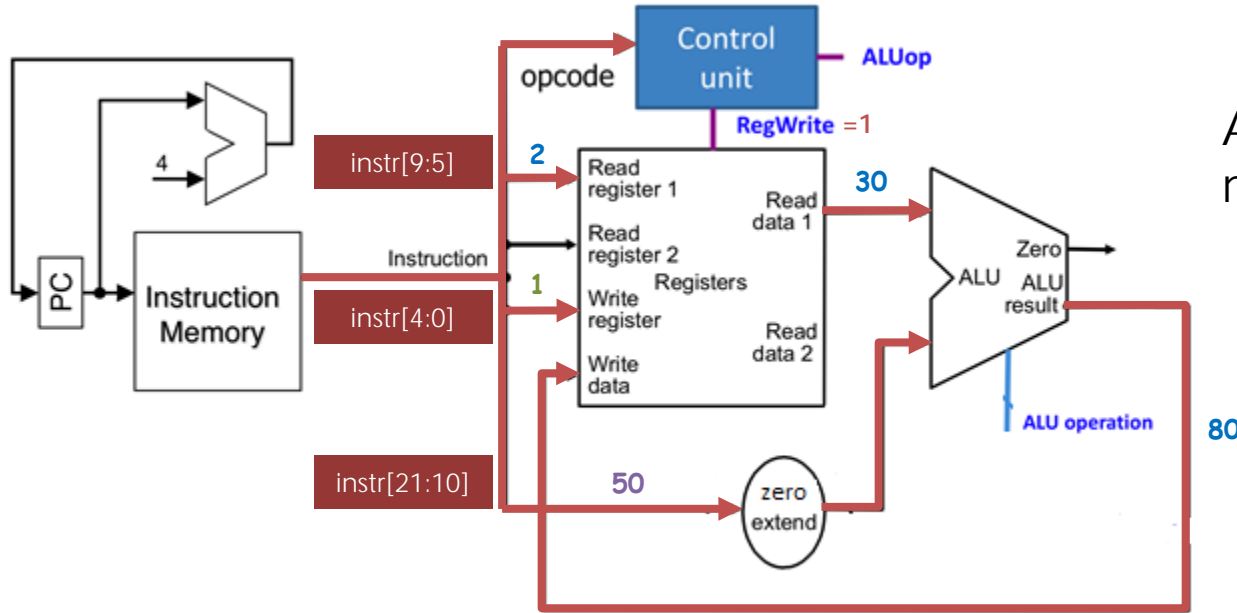


ADDI X1, X2, #50  
meaning( $[X1] \leftarrow [X2] + 50$ )

# Conditional Branch Instructions

 

- Read register (Rt) operands
- Compare operands according to condition
  - For CBZ (Use ALU, and check Zero output)
- Calculate target address
  - Sign-extend displacement for “address”
  - Shift left 2 places (word displacement)
  - Add to PC ( $PC + \text{sign extend}(\text{address}) \ll 2$ )
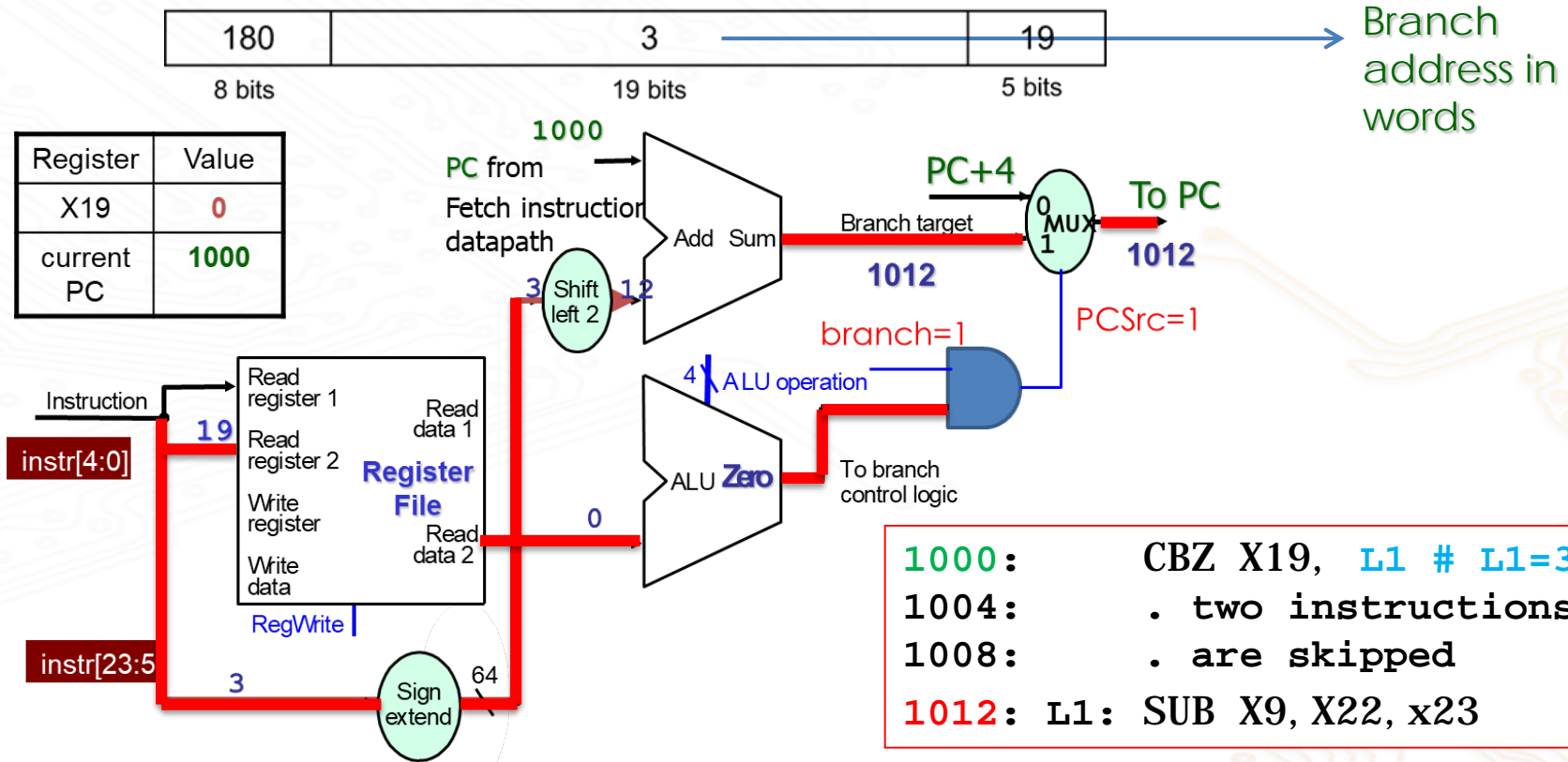
# Datapath for CB type – Branch instruction



# Datapath for R , D, I and CB type Instructions


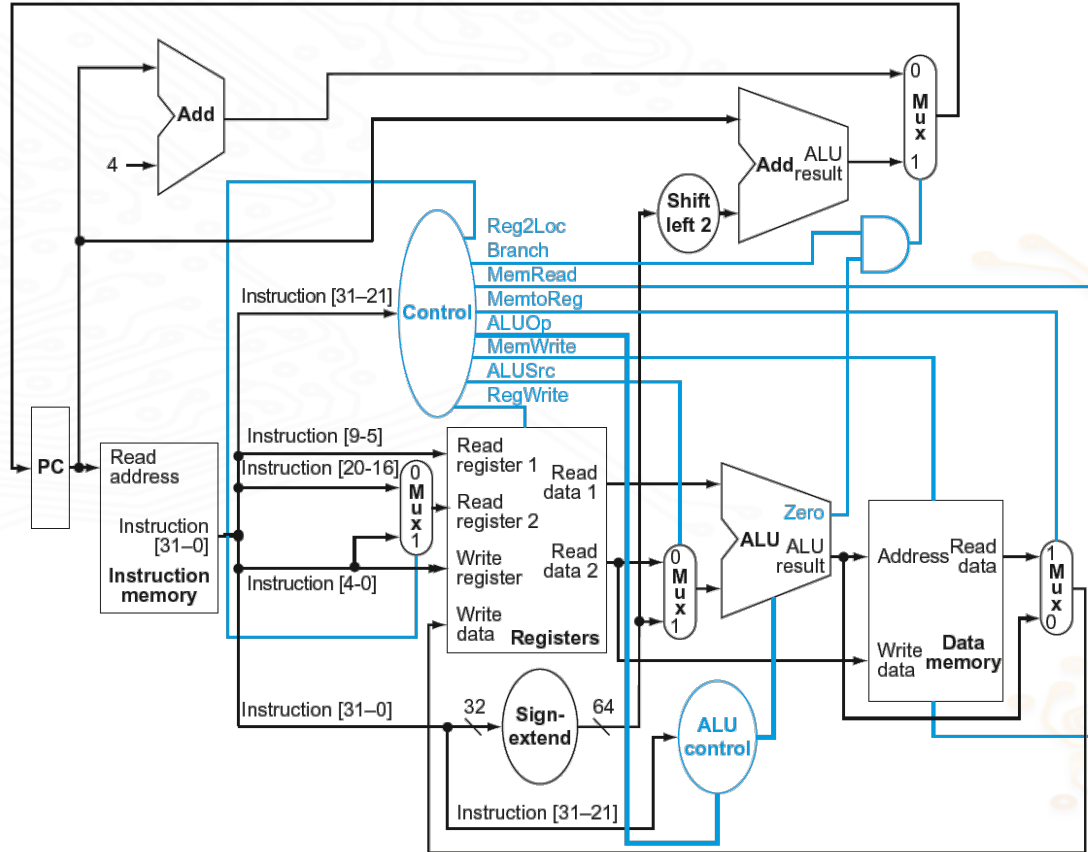



Figure 4.15, page 359 From Computer organization and design: the hardware/software interface ARM edition, by D. A. Patterson, J. L. Hennessy & P. Alexander, 2017 Amsterdam: Morgan Kaufmann.

# R-type datapath

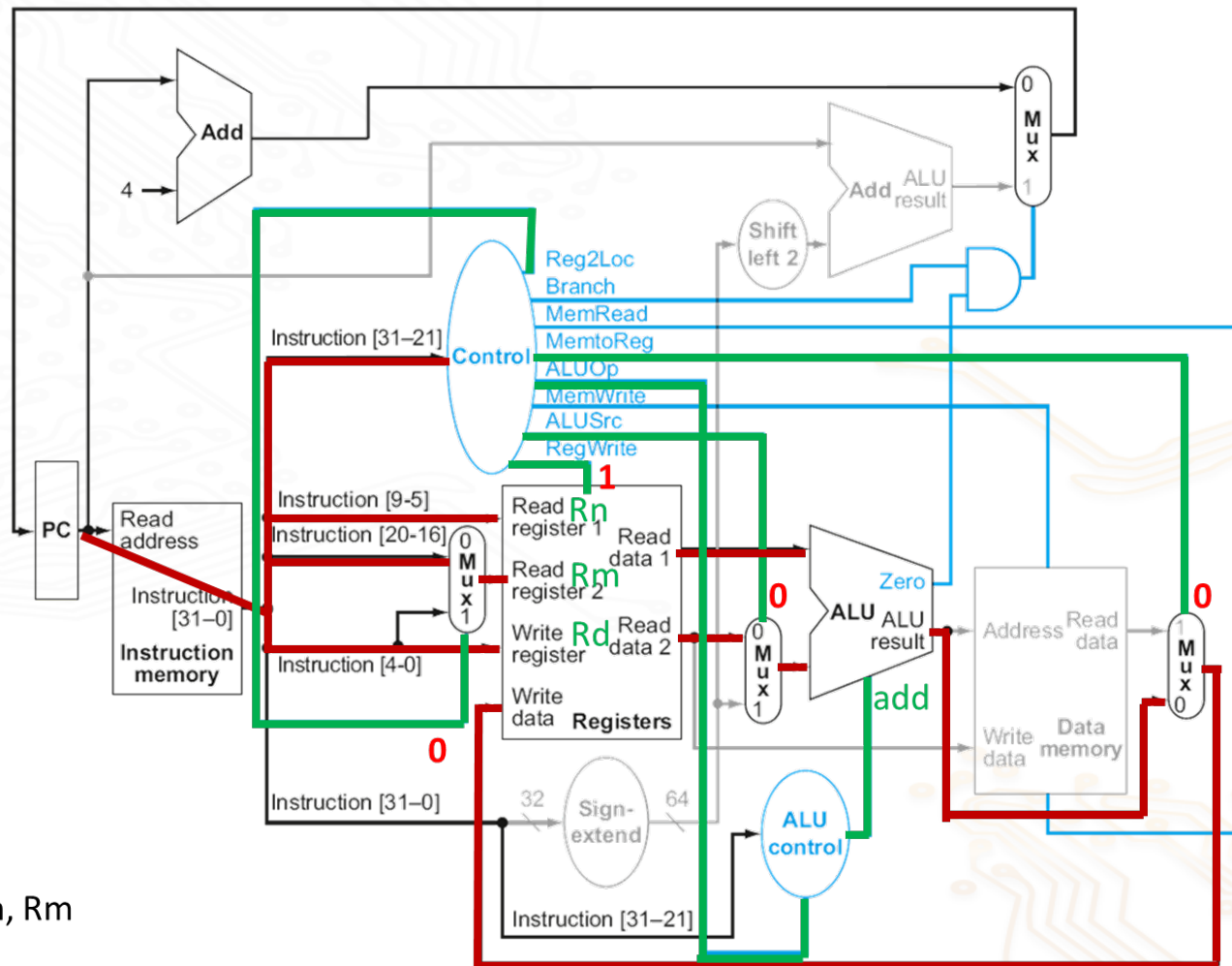


example: ADD Rd, Rn, Rm

Load  
(D-type)  
datapath

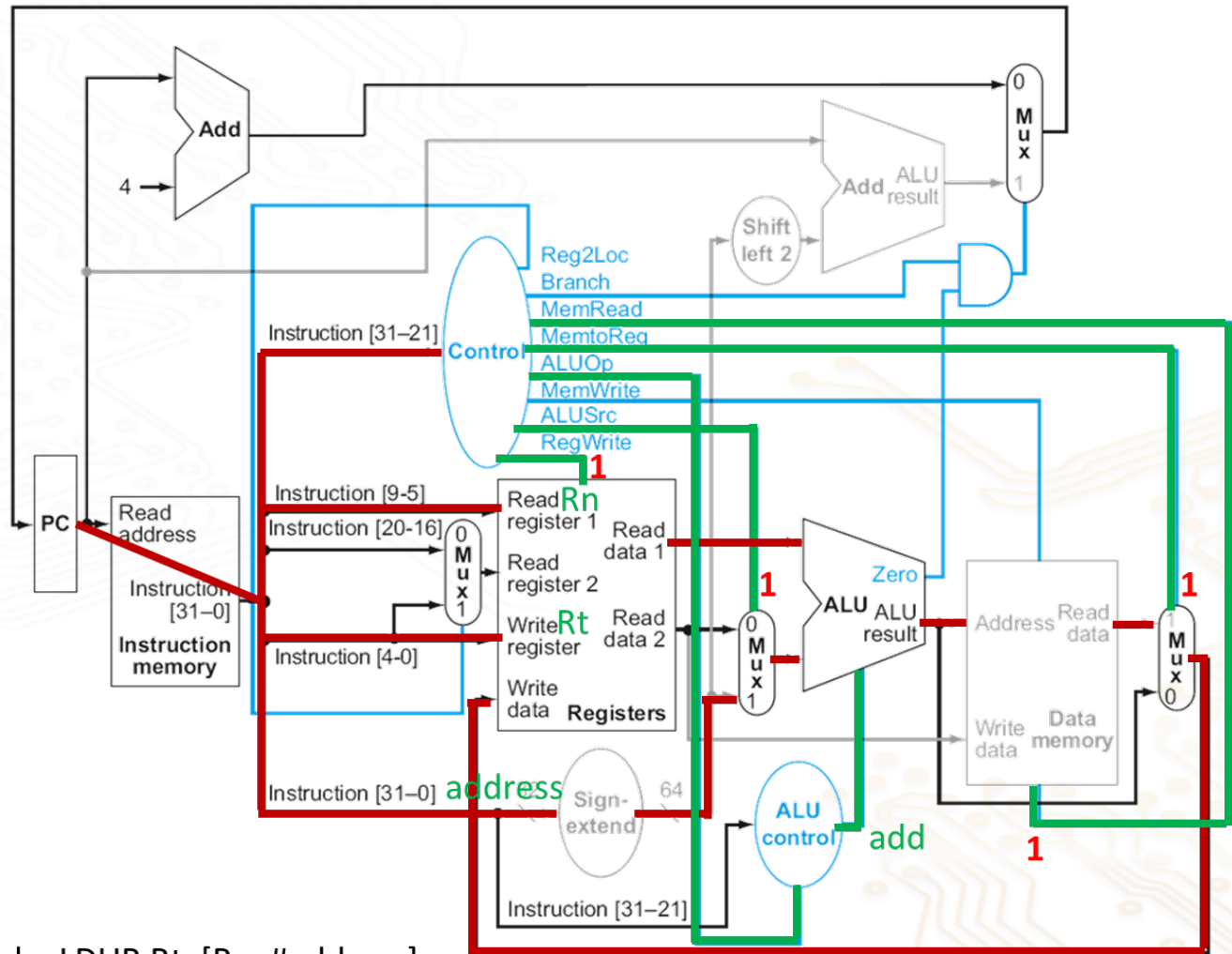


Example: LDUR Rt, [Rn, #address]

CBZ  
(CB-type)  
datapath

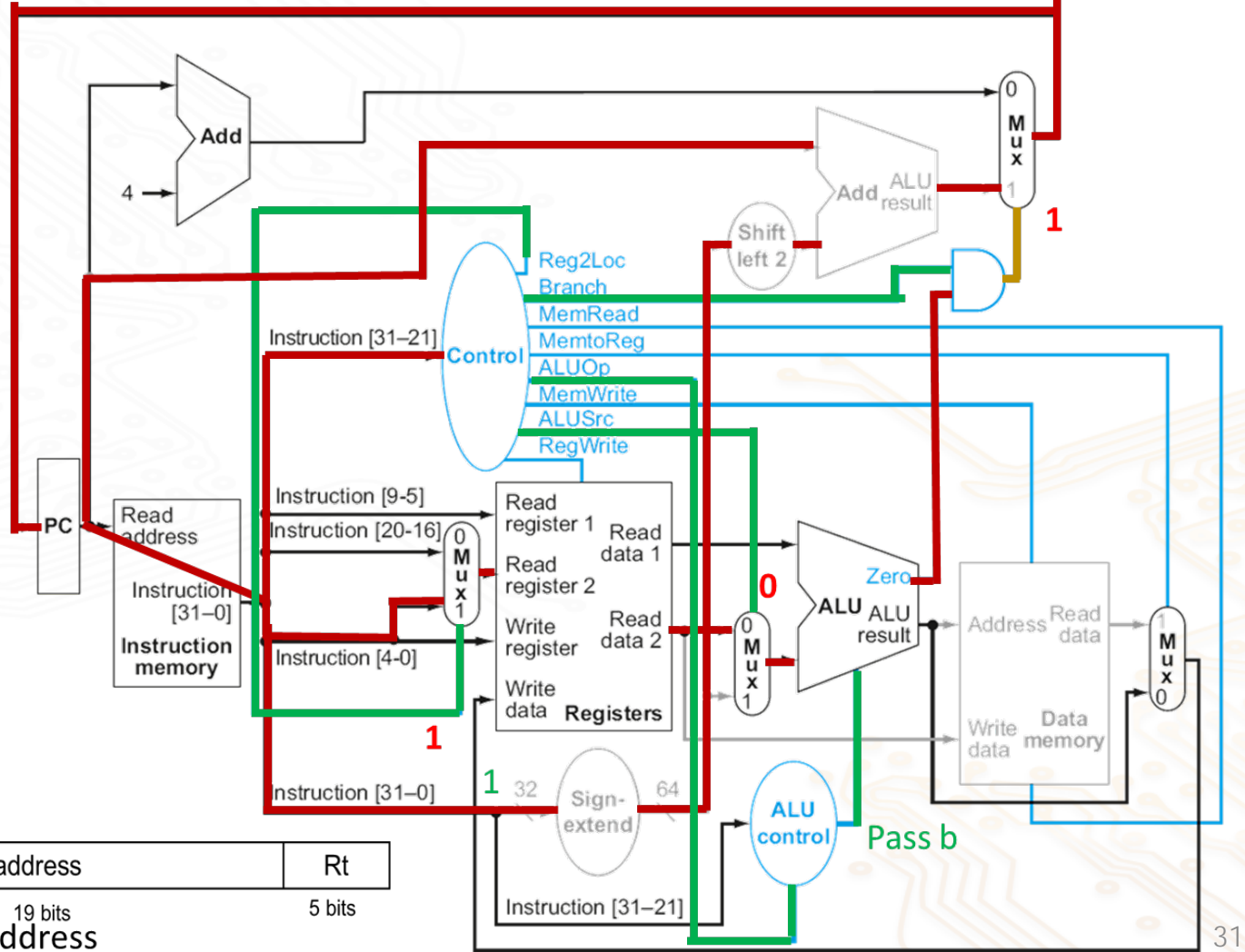

 
# Implementing Un-Conditional Branch Instructions



- Branch uses word address
  - 26-bit unconditional Branch address
  - Left shift by 2 (or add "00" to LSB)
  - Add with PC
- Need an extra control signal decoded from opcode


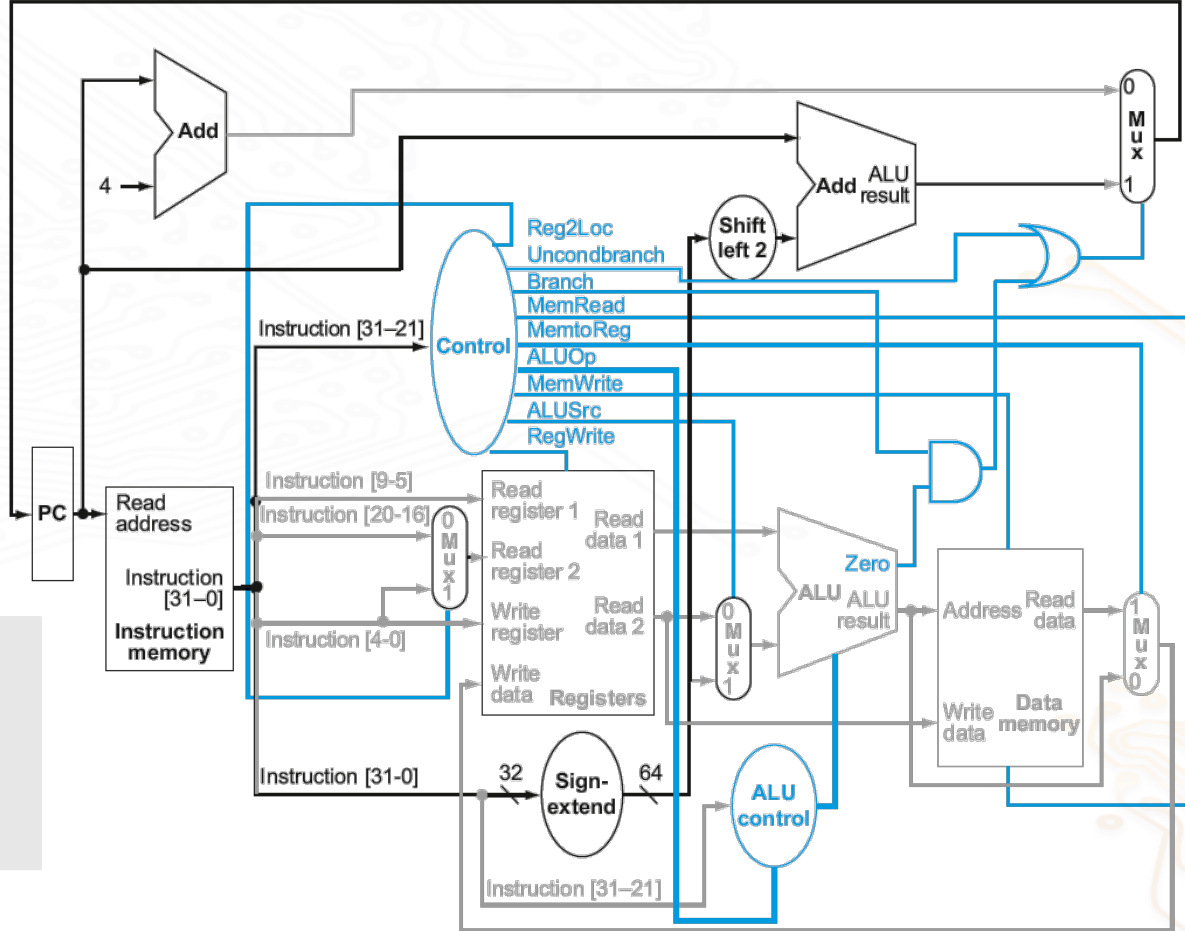
# Complete Datapath including B Instructions



B  
(B-type)  
datapath

# Summary of creating an architecture

- Combine all into a single architecture
  - Using mux with control signals
- Five steps finishes in a single clock cycle
  - Step 1: Instruction Fetch
  - Step 2: Instruction Decode and Register Fetch
  - Step 3: Execution, Memory Address Computation, or Branch Completion
  - Step 4: Memory Access or R-type instruction completion
  - Step 5: Write-back step
- No functional unit can be used twice in one clock cycle
- The clock period is decided by the slowest instruction

# Performance issue of single cycle architecture

- Longest delay determines clock period
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
  - Making the common case fast
- **improve performance by pipelining**